

Registration No.:

Course Code: ECE249

Course Title: BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

Max 1

Time Allowed: 3hrs.

Read the following instructions carefully before attempting the question paper.

1. Match the Paper Code shaded on the OMR Sheet with the Paper code mentioned on the question paper and ensure that both are same.
2. This question paper is divided into two parts A and B.
3. Part A contains 30 questions of 1 mark each. 0.25 marks will be deducted for each wrong answer.
4. Part B contains 5 questions of 10 marks each. Attempt any 4 questions out of these 5 questions. In case all the 5 questions are then only the first four attempted questions will be evaluated.
5. Attempt all the questions in serial order.
6. Do not write or mark anything on the question paper except your registration no. on the designated space.
7. After completion of first 90 minutes, the OMR sheet will be taken by the invigilator.
8. Submit the question paper and the rough sheet(s) along with the answer sheet to the invigilator before leaving the examination.

Part-A

Q1)

(1) If Set and Reset, both are disabled in case of SR flip flop then output is _____

- (a) Reset (b) Set (c) Previous output (d) Previous input

(2) Each stage of Shift register is capable of storing _____

- (a) 1 bit (b) 1 byte (c) 2 bit (d) 2 byte

(3) Synchronous counter is also called _____

- (a) asynchronous counter (b) parallel counter (c) trip counter (d) tripple counter

(4) Identify the basic building block of Shift registers _____

- (a) T flip flop (b) SR flip flop (c) JK flip flop (d) D flip flop

(5) Shift counter is also known as _____

- (a) Johnson counter (b) Ripple counter (c) synchronous counter (d) Asynchronous counter

(6) The arrow direction in the diode symbol indicates _____

- (a) Direction of electron flow.
(b) Direction of hole flow (Direction of conventional current)
(c) Opposite to the direction of hole flow
(d) None of the above

(7) A semiconductor is formed by _____ bonds.

- (a) Covalent (b) Electrovalent (c) Co-ordinate (d) None of the above

(8) A semiconductor has _____ temperature coefficient of resistance.

- (a) Positive (b) Zero (c) Negative (d) None of the above

(9) Which region is heavily doped in case of BJT.

- (a) Collector (b) Base (c) Emitter (d) Gate

(10) The input resistance of common base BJT is of the order of:
(a) 100 ohm (b) 1000 ohm (c) 10 ohm (d) 1 ohm

(11) MOSFET is ideal for:
(a) Low switching frequency (b) High switching frequency
(c) Low voltage applications (d) medium voltage applications

high switching frequency

(12) Which of the following does not belong to MOSFET?
(a) Drain (b) Gate (c) Base (d) Source

(13) Which of the following is universal GATE?
(a) NOR (b) XOR (c) EXOR (d) OR

(14) Simplify $A(A+B)$
(a) AB (b) 1 (c) $(1+AB)$ (d) A

absorption law

(15) The output will be a LOW for any case when one or more inputs are zero in a/an
(a) OR Gate (b) NOT Gate (c) AND Gate (d) NAND Gate

(16) A decoder converts n inputs to outputs.
(a) n (b) 2^n (c) $n+1$ (d) 2^{n+1}

(17) Which of the following can be represented for decoder?
(a) Sequential circuit (b) Combinational circuit (c) Logical circuit (d) None of the mentioned

(18) The standard TTL gates are marketed as series.
(a) 80 (b) 82 (c) 74 (d) 08

(19) CMOS gates are commercially available as which of the following series?
(a) 1000 (b) 3000 (c) 2000 (d) 4000

(20) Which logic gate has low power consumption?
(a) RTL (b) TTL (c) DTL (d) CMOS

(21) Latch can be called Memory device as it has the capability of
(a) storing 1-bit (b) storing 1-byte (c) storing 16-bit (d) storing 24-bit

(22) R indicates in SR-latch.
(a) Re-arrange (b) Reset (c) Recombine (d) Residue

(23) The number of input in case of D-flip flop is/are:
(a) 1 (b) 3 (c) 2 (d) 4

(24) Identify the flip flop which can be used to make D-flip flop
(a) JK (b) SR (c) T (d) MS

Q8 & Q9

CO5, 15

Present input and Past output

CO5, 15

Q25) The output of sequential circuit depends on
(a) Present input (b) Past output (c) Present and Past output

CO5, 15

Q26) Which of the following logic expressions represents the logic diagram shown?
(a) $X = AB + AB$ (b) $X = (AB) + AB$ (c) $X = (AB) + A + B$ (d) $X = A + B + AB$

CO5, 15

Q27) 2-bit full adder contains
(a) 3 combinational inputs (b) 4 combinational inputs (c) 5 combinational inputs (d) 8 combinational inputs

CO5, 15

Q28) What is a multiplexer?
(a) It is a type of decoder which decodes several inputs and gives one output
(b) A multiplexer is a device which converts many signals into one
(c) It takes one input and results into many output
(d) It is a type of encoder which decodes several inputs and gives one output

CO5, 15

Q29) In parts of the processor, address are used to calculate
(a) Addresses (b) Table indices (c) Increment and decrement operators (d) All of the Mentioned

CO5, 15

Q30) Total number of inputs in a half adder is _____
(a) 2 (b) 3 (c) 4 (d) 1

Part-B

Q31) Explain: (i) Phase voltage and Line voltage (ii) rms value of ac signal with the help of relevant example
Q32) Explain the power calculation in RL, RC, and RLC circuits with the help of relevant example

CO2, L1, [10 marks]

Q33) Explain the working principle of DC motor. Write the different types of DC motor.
Q34) Explain single and three phase induction motors.

CO1, L2, [10 marks]

Q35) Explain intrinsic and extrinsic types of semiconductors, how n, p-type semiconductors are made? Explain majority, and minority charge carriers in both cases. Explain the donor and acceptor ions also.

CO1, L2, [10 marks]

Q36) Design full adder with half adders and full subtractor with half subtractors. you can use other required logic gates also.

CO4, L4, [10 marks]

Q37) Explain JK flip-flops in detail, along with their Truth-Table and logic diagram. Also, explain what is Race around condition and how can be avoided.

CO4, L4, [10 marks]

End of Question paper-

75-80%

4%

81-85%

6%

86%-90%

8%

90% -

10%

BMT

| AMT