
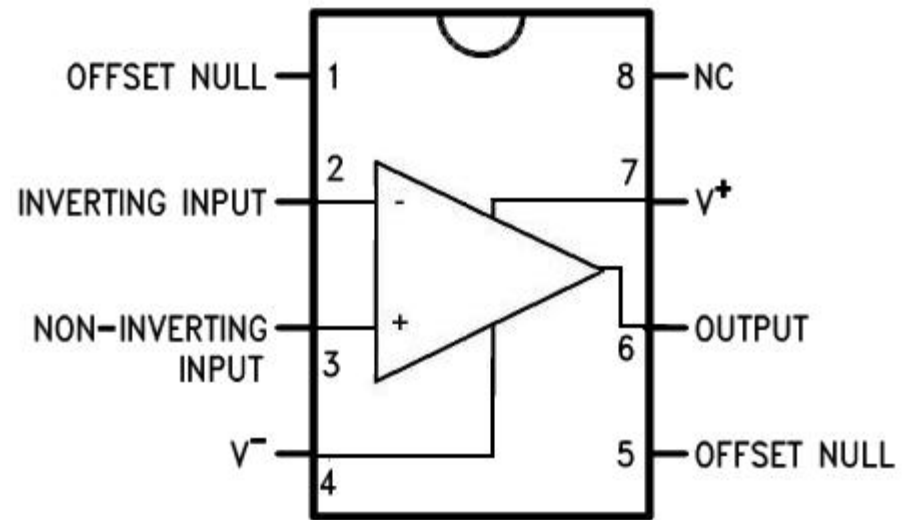


Unit-4:

OP-AMP

(Operational Amplifier)

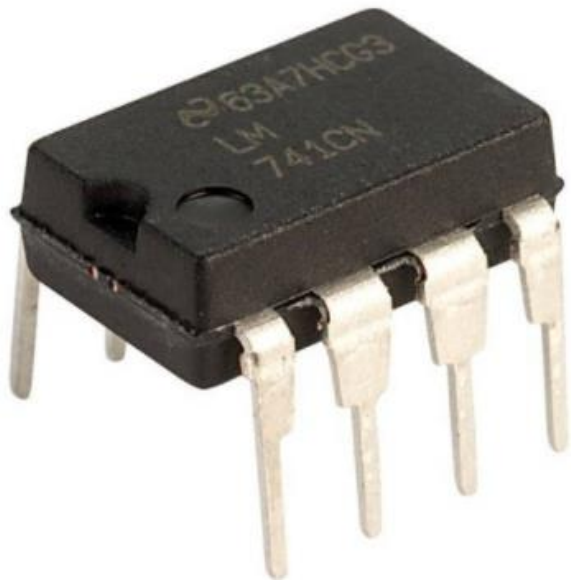

MCQ

In which of the following application op-amp is/are used?

- (a) Integrator and Differentiator
- (b) Voltage to Current Converter
- (c) Adder or Summing Amplifier
- (d) All of the above

Introduction

- OP-AMP is basically a multistage amplifier which uses a number of amplifier stages interconnected to each other.
- OP-AMP amplifies the difference between two signals and diminishes common signals.
- The integrated op amp offers all the advantages of monolithic integrated circuits such as small size, high reliability, reduced cost, less power consumption.

MCQ

Op-Amp is abbreviated as _____.



- (a) Operational Amplifier
- (b) Operand amplitude
- (c) Operational amplitude
- (d) None of the above

MCQ

The Op-amp can amplify

- (a) a.c. signals only
- (b) d.c. signals only
- (c) both a.c. and d.c. signals
- (d) neither d.c. nor a.c. signals

Symbol and terminals

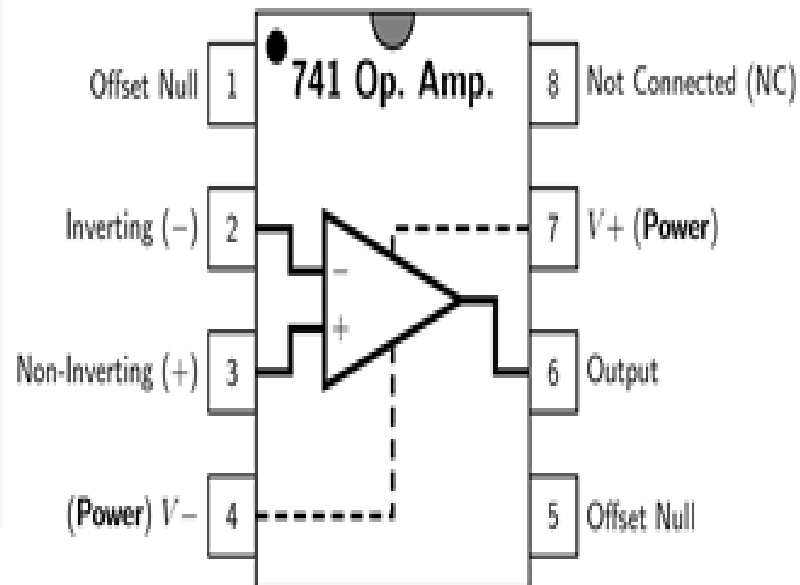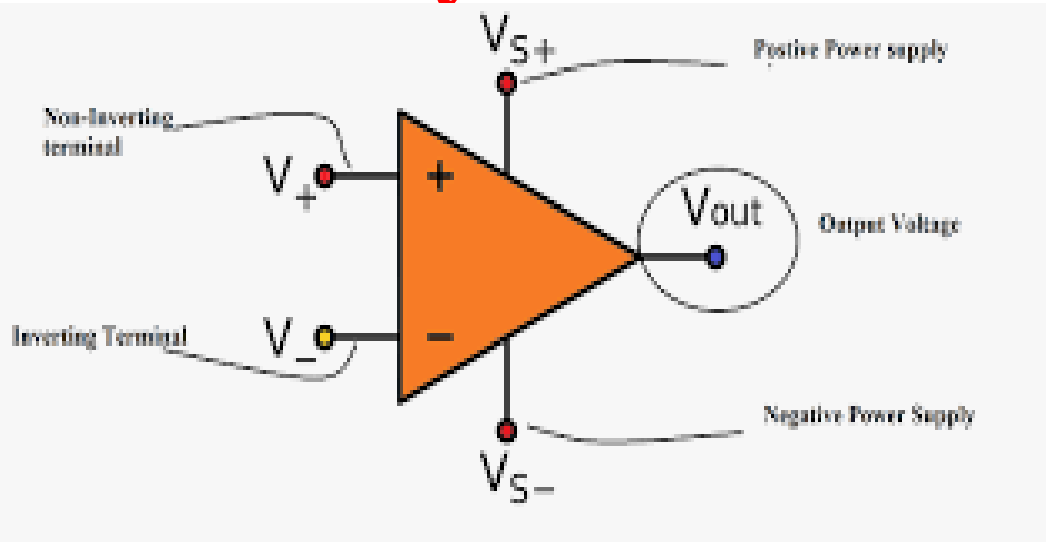


- An OP-AMP has a two input terminal, one output terminal and two supply voltage terminals.
- The input terminal marked with negative(-) sign is called as an **inverting terminal**.

If we connect the input signal to this terminal then the amplified output signal is 180° out of phase with respect to input.

- The input terminal marked with positive (+) sign is called as **Non-Inverting terminal**.

If the input is applied to this pin then the amplified output is in phase with the input.

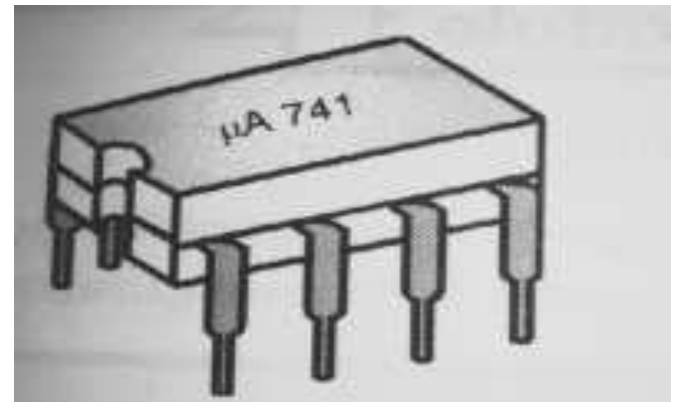- Offset null is used to nullify the offset voltage and pin no 8 is dummy pin.




MCQ

Op-Amp has _____ gain.


- (a) Low
- (b) High
- (c) Zero
- (d) Infinity

Inverting Amplifier

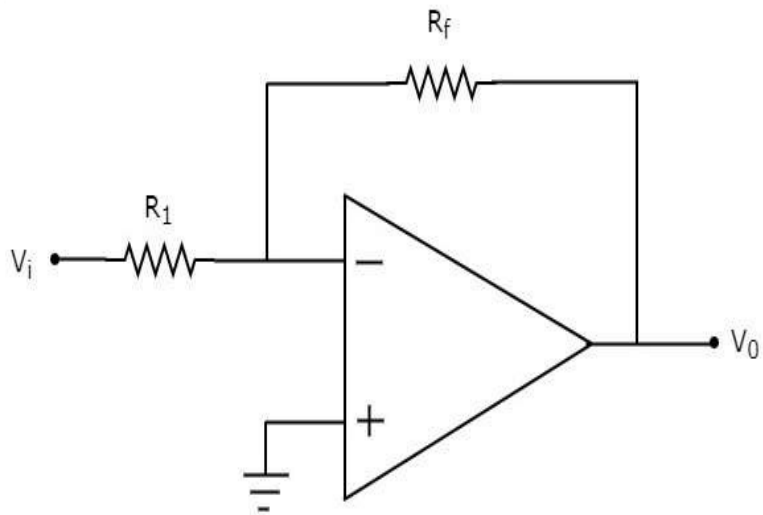

$$\frac{V_0}{V_i} = -\frac{R_f}{R_1}$$

Non-Inverting Amplifier

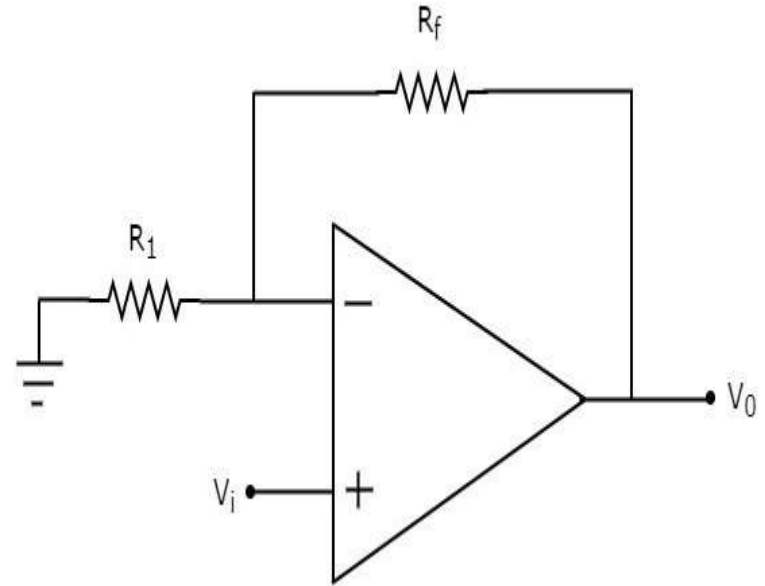

$$\frac{V_0}{V_i} = 1 + \frac{R_f}{R_1}$$

Characteristics of an OP-AMP

- Characteristics are important because, we can use them to compare the performance of various op amp ICs and select the best suitable from them for the required application.

characteristics	Practical value	Ideal value
Voltage gain	2×10^5	∞
Input resistance	$2\text{M}\Omega$	∞
Output resistance	75Ω	0
Bandwidth	1 MHz	∞
CMRR	90 dB	∞
Slew rates	$0.5\text{V}/\mu\text{s}$	∞
PSRR	$150\mu\text{V}/\text{V}$	0

MCQ

Which one of the following characteristics is true for ideal op-amp?

- (a) $R_i=0$
- (b) $R_o= \infty$
- (c) B.W.= 0
- (d) CMRR= ∞

MCQ

Which one of the following characteristics is not true for ideal op-amp?


- (a) $R_i = \infty$
- (b) $R_o = 0$
- (c) B.W. = 0
- (d) Gain = ∞

MCQ

Which one of the following combination for op-amp characteristics is true ?

- (a) $R_i = \infty$, Voltage gain = 0
- (b) $R_o = 0$, CMRR = ∞
- (c) B.W. = 0, Voltage Gain = 0
- (d) Gain = ∞ , Slew Rate = 0

Concept of virtual short

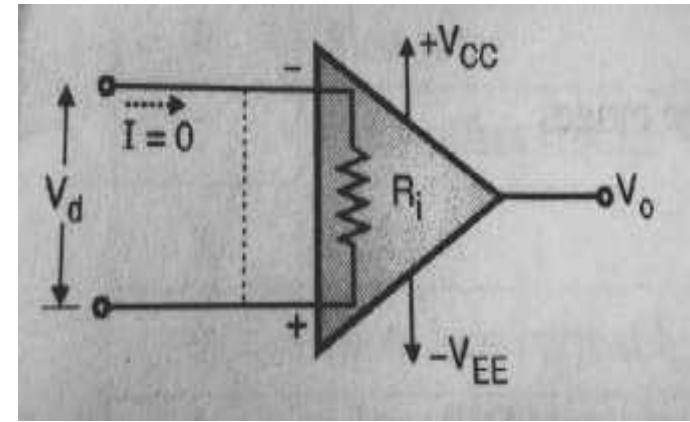

- The input impedance of an OP-AMP is ideally infinite. Hence current flowing from one input terminal to the other will be zero.
- Thus the voltage drop across R_i will be zero and both the terminals will be at the same potential.
- Means they are virtually shorted to each other

Virtual Ground

If one of the terminal of OP-AMP is connected to ground then due to the virtual short existing between the other input terminal, the other terminal is said to be at ground potential.

