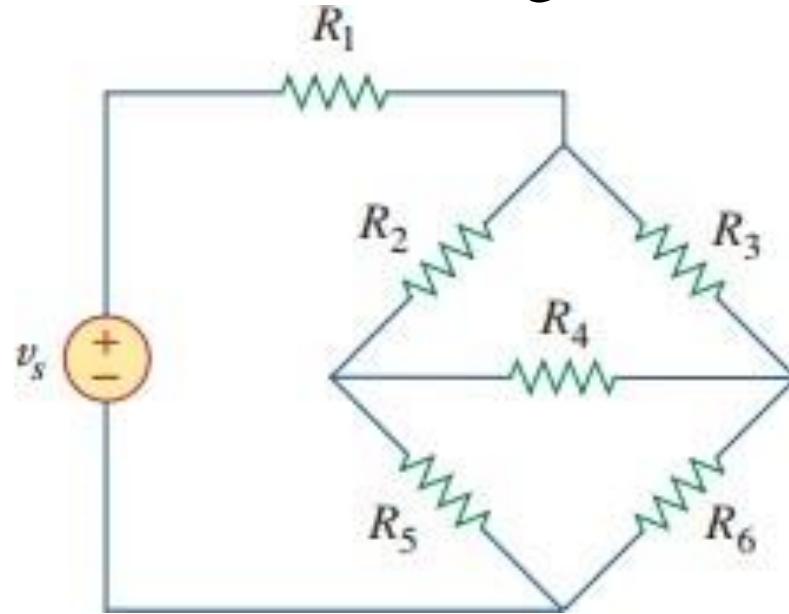


# UNIT 1: DC CIRCUITS

Lecture 4 and 5

# Star Delta Transformation

- Situations often arise in circuit analysis when the resistors are neither in parallel nor in series. For example, consider the bridge shown in the figure.





# Star Delta Transformation



There are two types of such circuits

1. Star Connection
2. Delta Connection

**STAR**

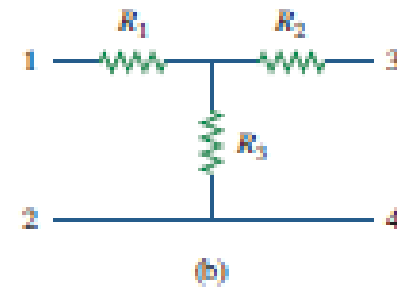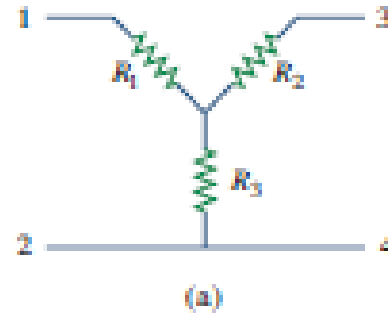

**DELTA**

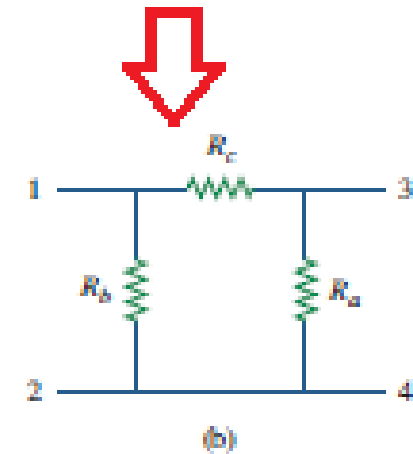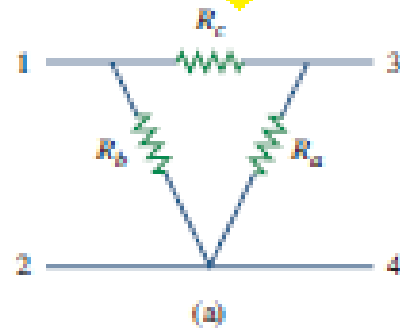


# Delta to Star Conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
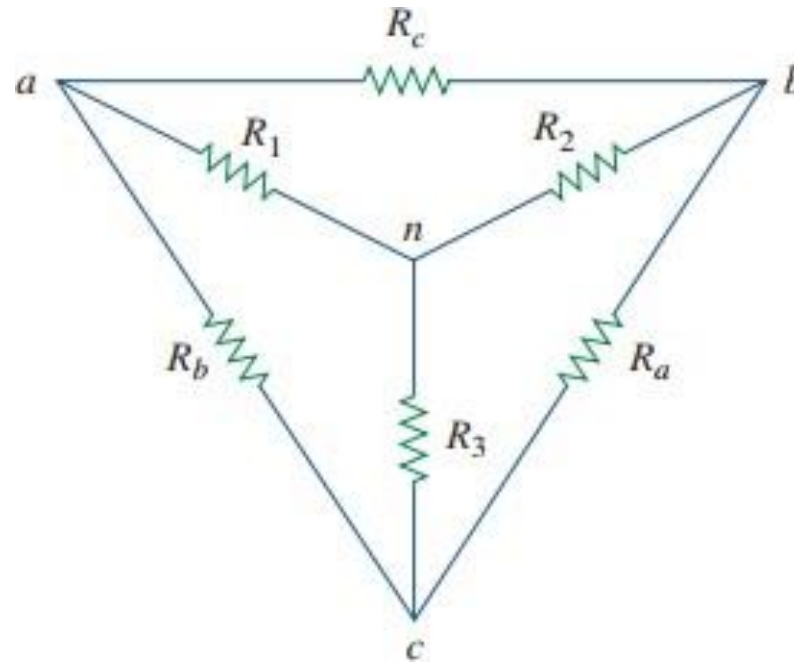
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$




# Star to Delta Conversion

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
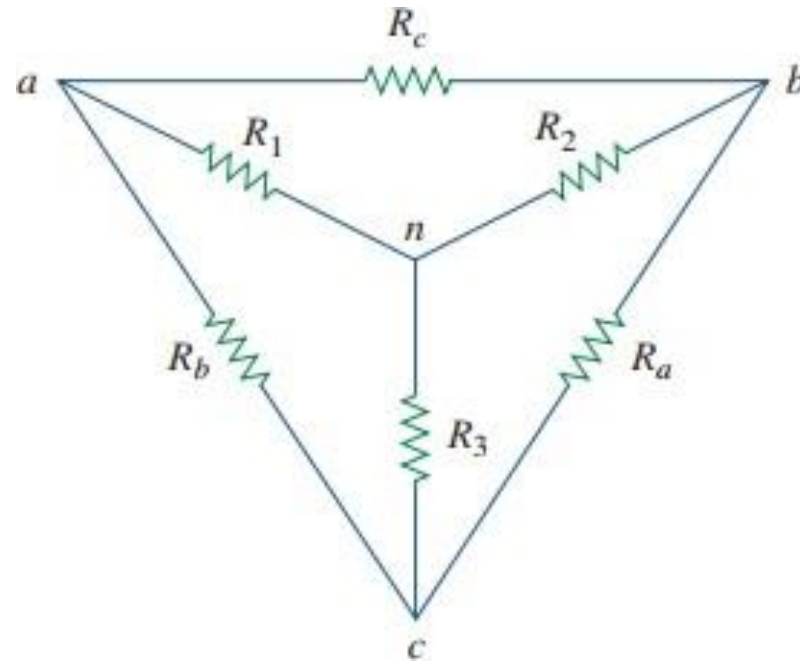
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


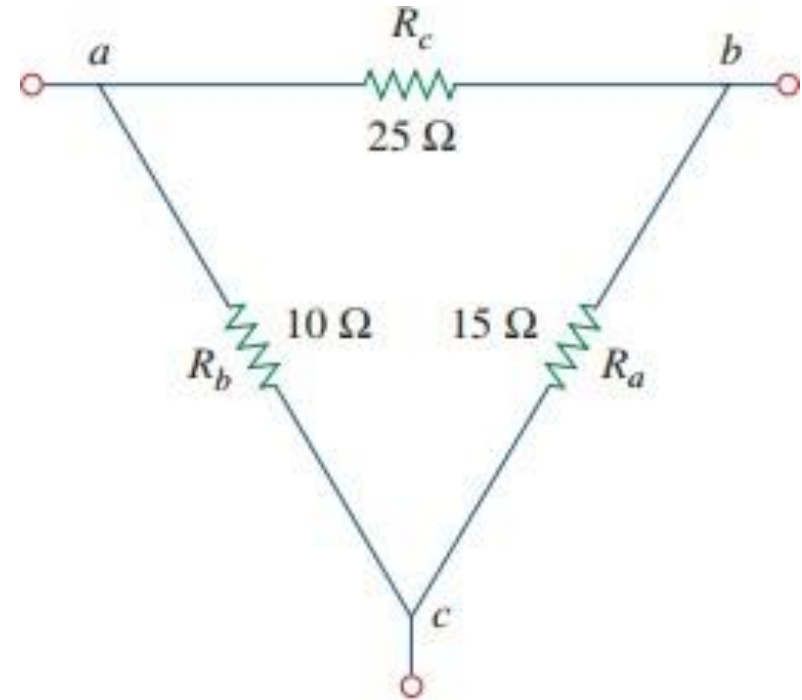
# Practice Problem

Q: Convert  $\Delta$  network into a  $Y$  network?




# Practice Problem

Q: Convert  $\Delta$  network into a Y network?

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{10 \times 25}{15 + 10 + 25} = \frac{250}{50} = 5 \Omega$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{25 \times 15}{50} = 7.5 \Omega$$

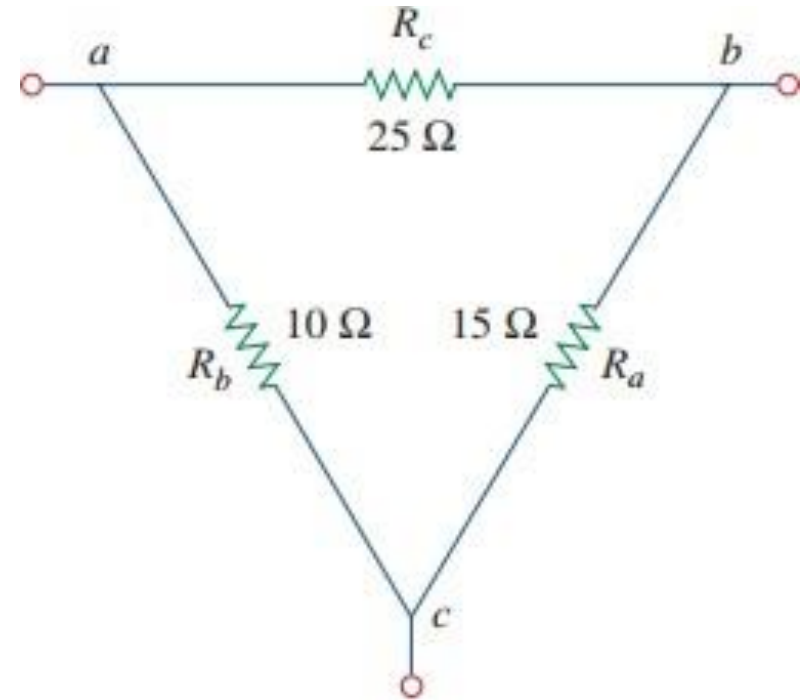
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 10}{50} = 3 \Omega$$



# QUICK QUIZ (Poll 1)

Resistance  $R_{bc}$  for the  $\Delta$  network of the corresponding Figure is:

- A. 140
- B. 70
- C. 35
- D. 100

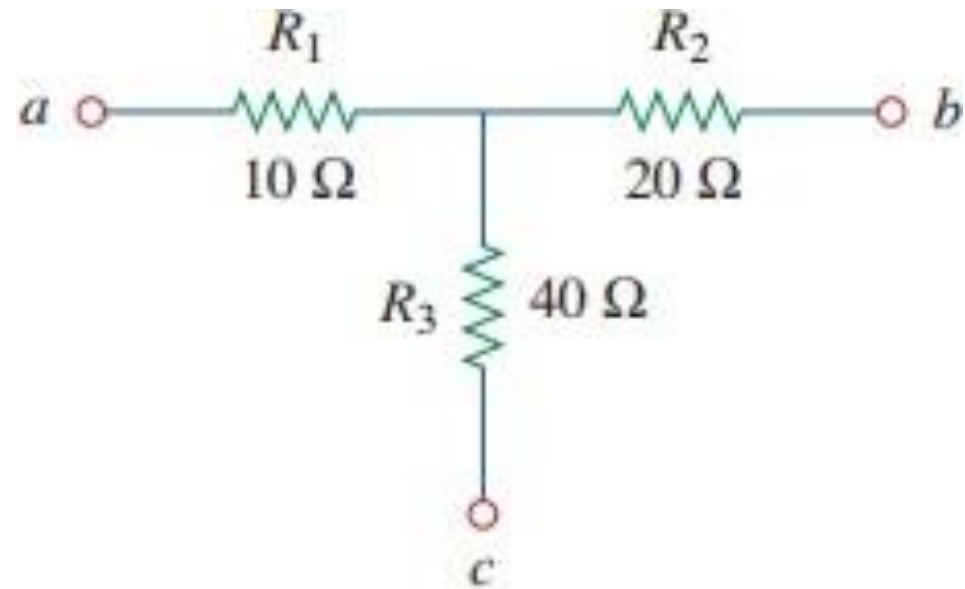





# QUICK QUIZ (Poll 2)

Q: If  $R_a = R_b = R_c = R$  in a  $\Delta$  network, then  $R_1 = R_2 = R_3 = ?$

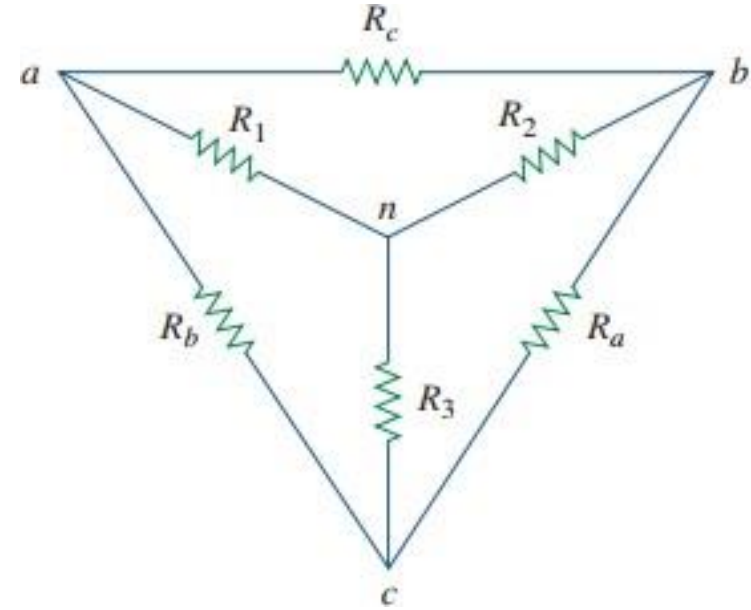- A.  $3R$
- B.  $R/3$
- C.  $R$
- D.  $R/2$



# Energy Sources

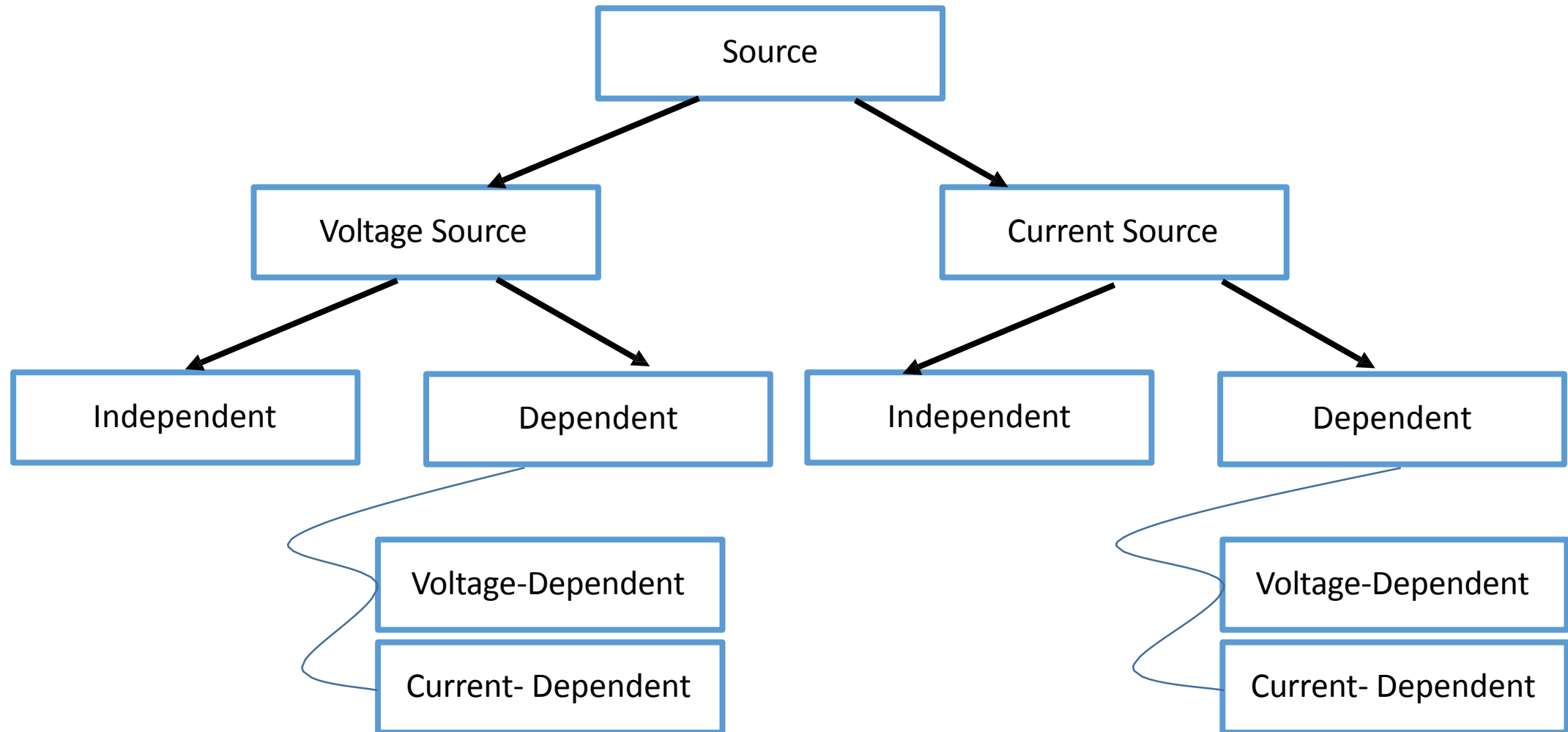


# Independent and Dependent Sources


- **Independent sources** are those which **does not depend on any other quantity** in the circuit. They are two terminal devices and has a **constant value**, i.e. the voltage across the two terminals remains constant **irrespective of all circuit conditions**. The Independent sources are represented by a **circular shape**.
- **Dependent or Controlled** sources are those whose **output voltage or current is NOT fixed** but depends on the voltage or current in **another part** of the circuit. When the strength of voltage or current changes in the source for any change in the **connected network**, they are called dependent sources. The dependent sources are represented by a **diamond shape**.

# Independent and Dependent Sources

- Independent

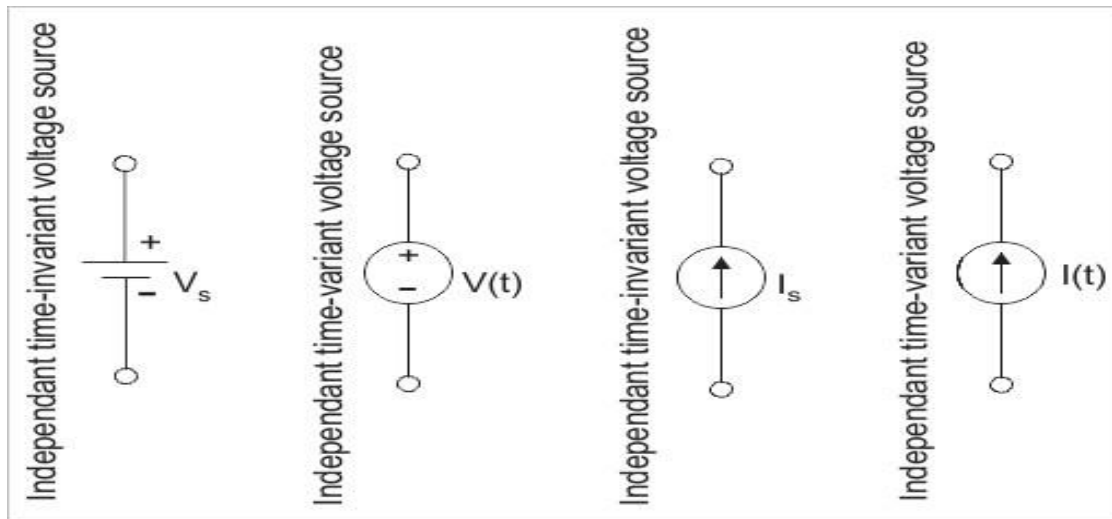

- Dependent

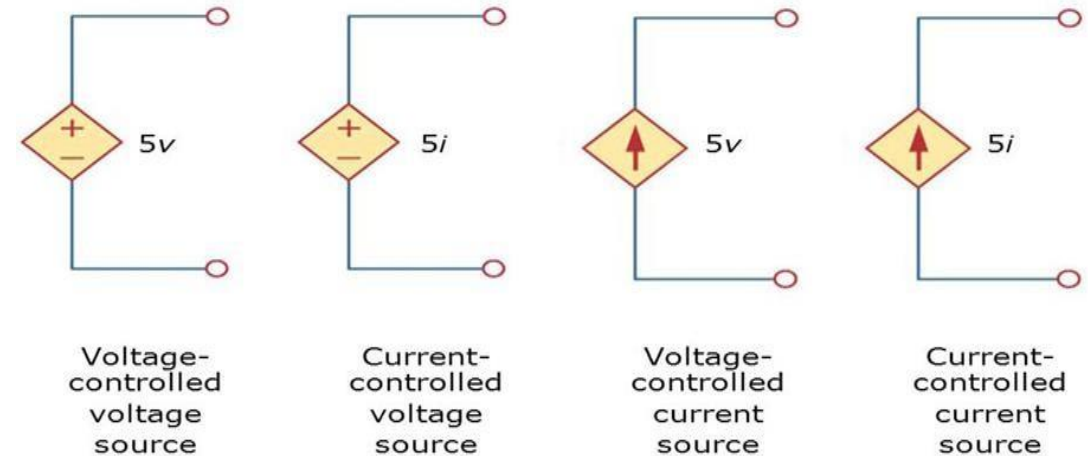

# Ideal and Practical Voltage Source

- Ideal is one where internal resistance does NOT exist. NOTE:
  1. For a voltage source, internal resistance must be ZERO.
  2. For a current source, internal resistance must be INFINITY.
- Practical is one where internal resistance is present.

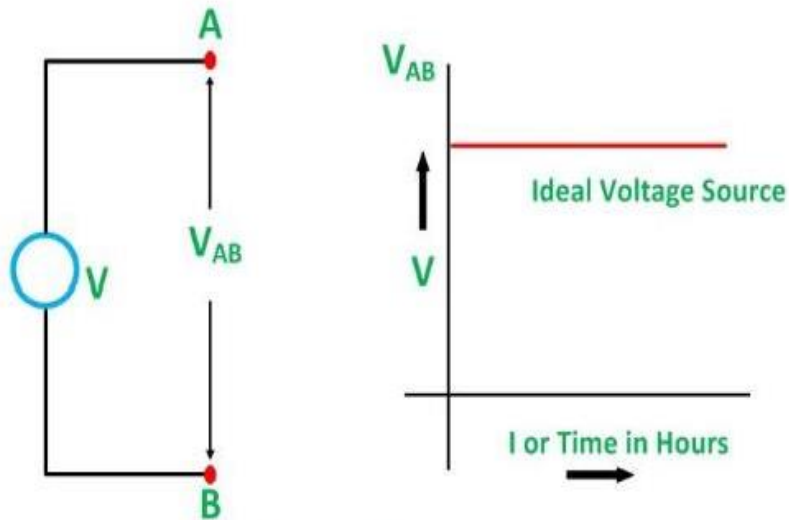


Figure A

Circuit Globe

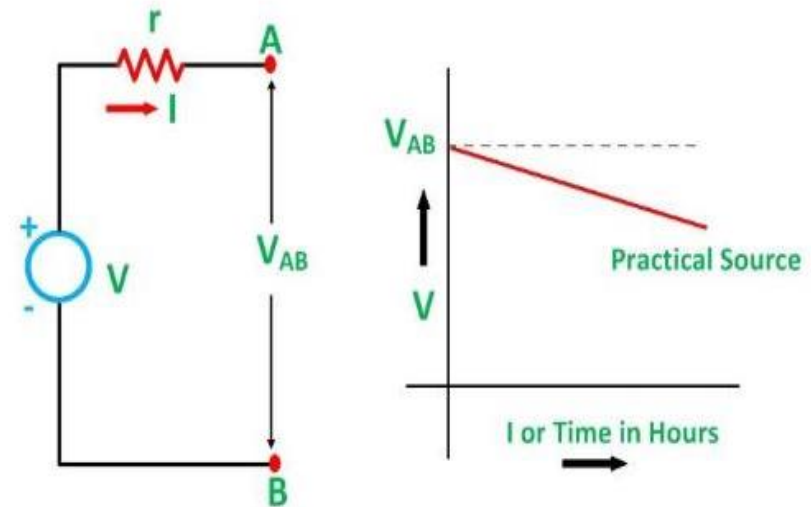


Figure B

Circuit Globe

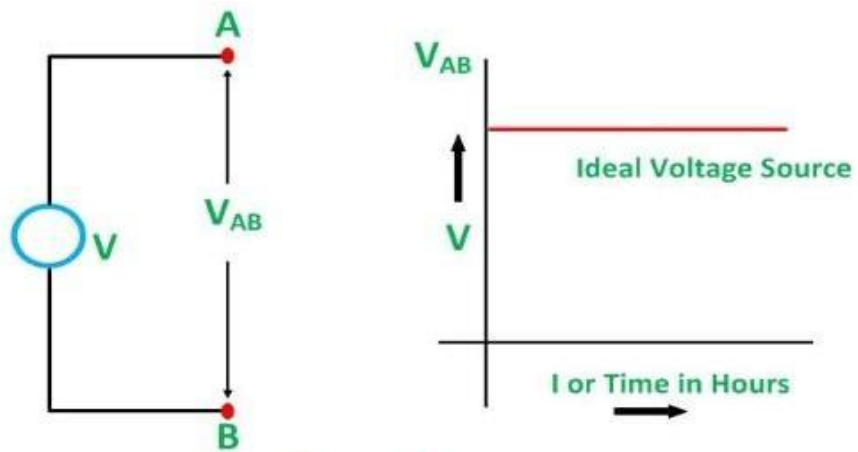


Figure A

Circuit Globe

The figure B shown below gives the circuit diagram and characteristics of Practical Voltage Source

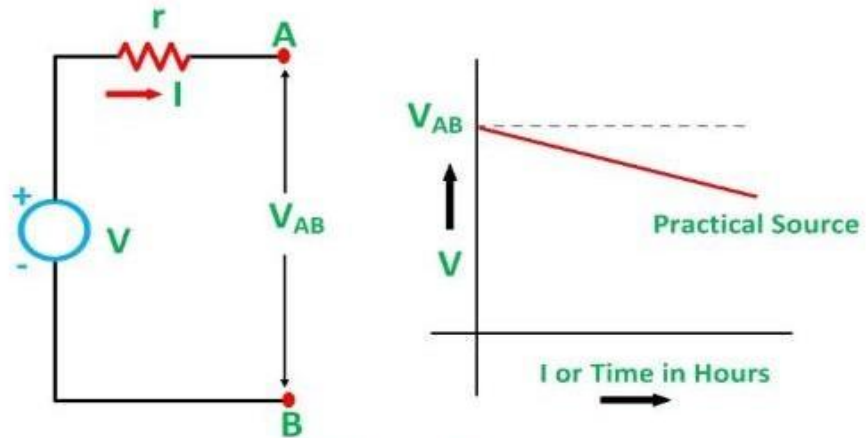


Figure B

Circuit Globe

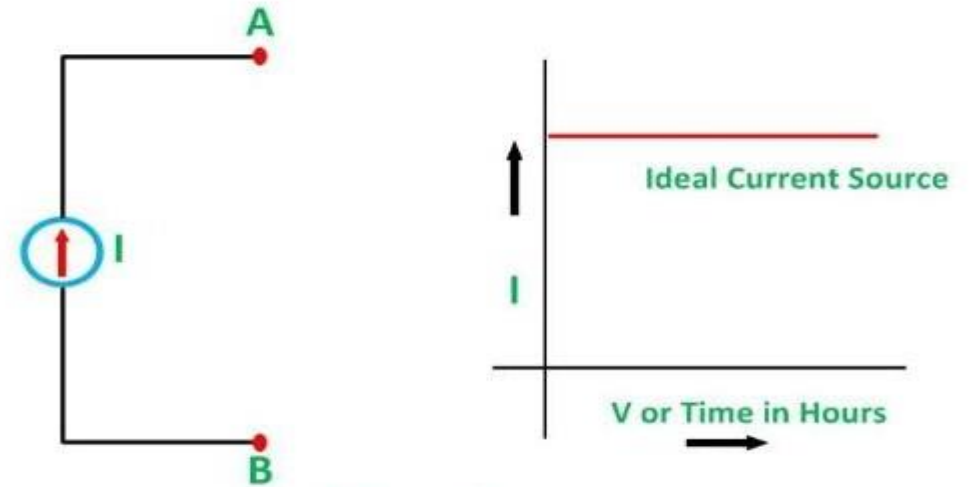


Figure C

Circuit Globe

Figure D shown below shows the characteristics of Practical Current Source.

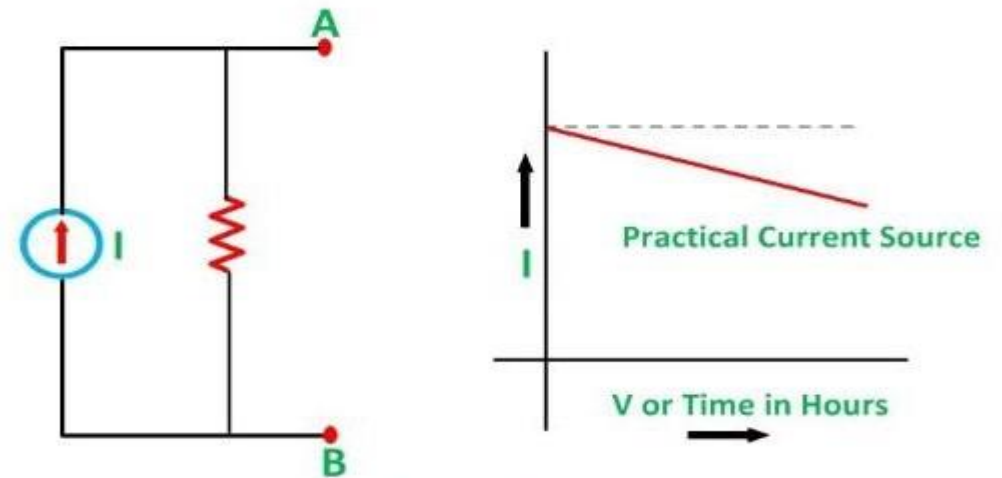



Figure D

Circuit Globe

# QUICK QUIZ (Poll 3)

Identify the type of dependent source used in the network:

- A. VCVS
- B. CCCS
- C. VCCS
- D. CCVS

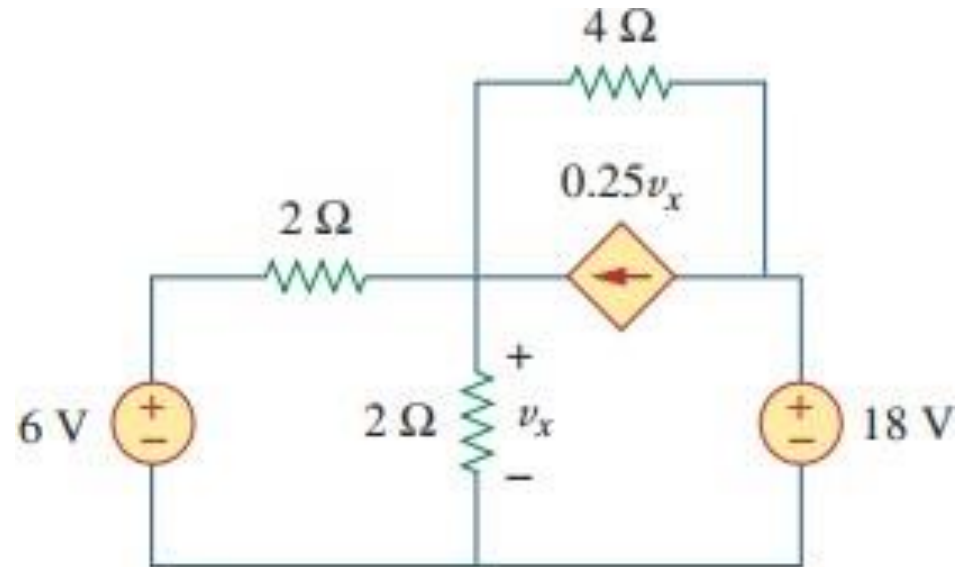

# Nodal Analysis


- Nodal analysis provides a general procedure for analyzing circuits using **node voltages** as the circuit variables.
- Choosing node voltages instead of element voltages as circuit variables is convenient and reduces the number of equations one must solve simultaneously.
- Applicable to **nodes** only.
- It is used to find the **unknown node voltages**.
- This Method is Application of **KCL**+Ohm's Law Only



# Steps to Determine Node Voltages

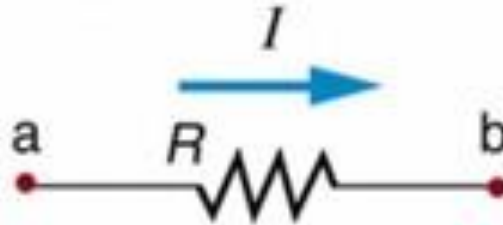1. Select **one** nodes out of 'n' node as the **reference node**. Assign voltages to the **remaining nodes**. The voltages are referenced with respect to the reference node.
2. **Apply KCL** to each of the non-reference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. **Solve the resulting simultaneous equations** to obtain the unknown node voltages.

- The number of non-reference nodes is **equal** to the number of **independent equations** that we have to derive.
- Current flows from a **higher potential to a lower potential** in a resistor



$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$

# QUICK QUIZ

For “N” number of nodes, the number of non-reference nodes is equal to:

- A.  $N + 1$
- B.  $N - 1$
- C.  $2N$
- D.  $2N - 1$

# QUICK QUIZ


Nodal analysis, which is based on KCL is used to find unknown:

*A. current*

*B. voltage*
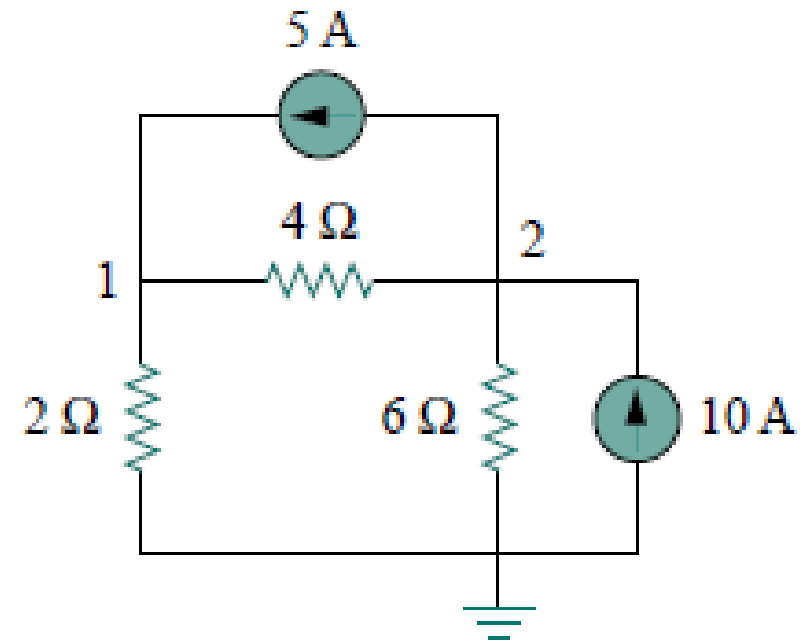
# Example 1

- Obtain the node voltages in the given circuit?



# Mesh Analysis

- Mesh analysis provides another general procedure for analyzing circuits, using **mesh currents** as the circuit variables.
- It is based on **KVL**.



## RECALL!

- **LOOP:** A loop is a closed path with no node passed more than once.
- **MESH:** A mesh is a loop that does not contain any other loop within it.
- Mesh analysis is not quite as general as nodal analysis because it is only applicable to a circuit that is **planar**.
- **PLANAR CIRCUIT:** A planar circuit is one that can be drawn in a plane **with no branches crossing one another**; otherwise it is nonplanar.

# Steps to Determine Mesh Currents

1. Assign mesh currents to 'n' meshes
2. Apply **KVL** to each of the 'n' meshes.
3. **Solve the resulting 'n' simultaneous equations** to obtain the unknown mesh currents.

# Examples of Planar Circuits

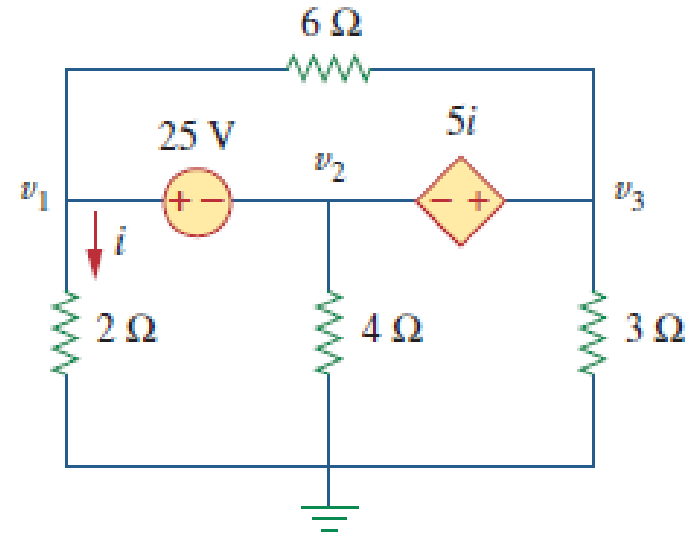
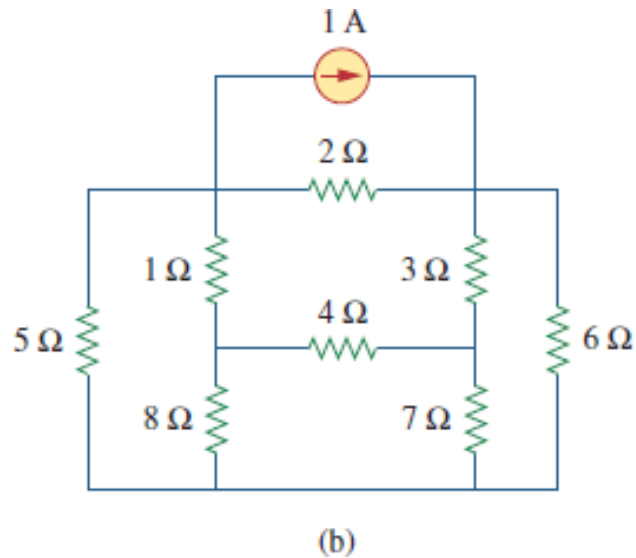


NOTE: A **mesh** is a loop which does not contain any other loops within it.

Mesh Analysis can be applied to meshes only inside the circuit, **Not to LOOP**.



# Examples of Non-Planar Circuits

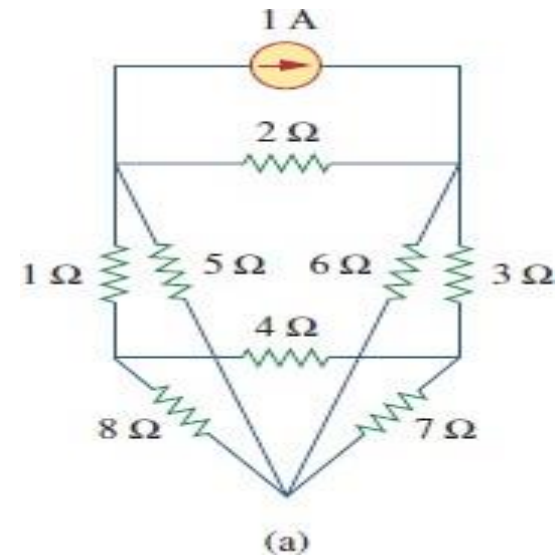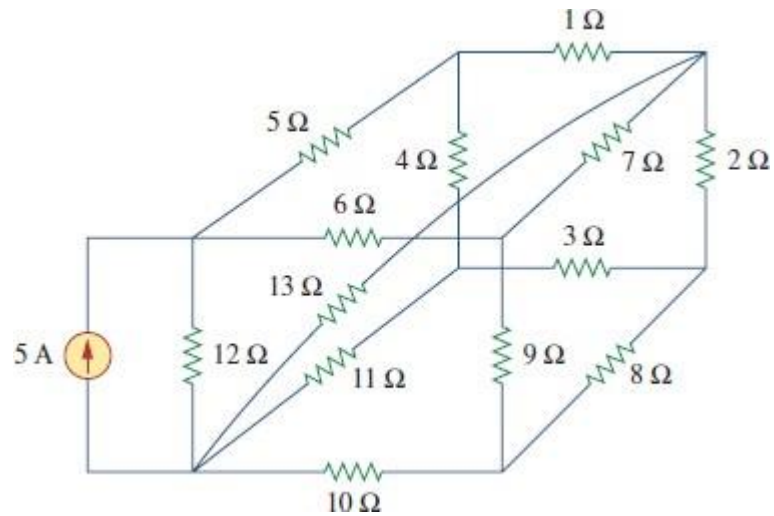

# QUICK QUIZ

Mesh Analysis is applicable to \_\_\_\_\_ type networks.:

- A. Planar and Loop
- B. Non planar and mesh
- C. Planar and mesh
- D. Non planar and Loop

# QUICK QUIZ

Mesh analysis, which is based on KVL is used to find unknown:

A. *current*

B. *voltage*

# Example 1

- Obtain the mesh currents in the given circuit?

