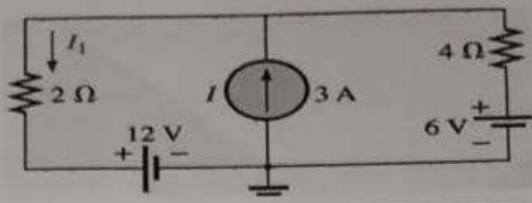
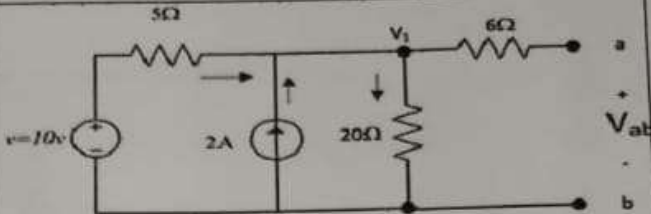
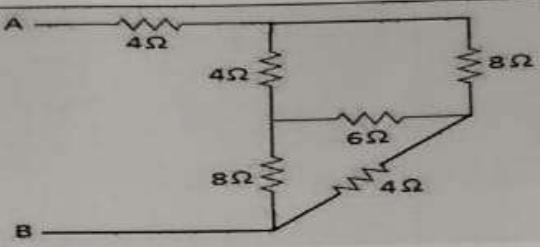
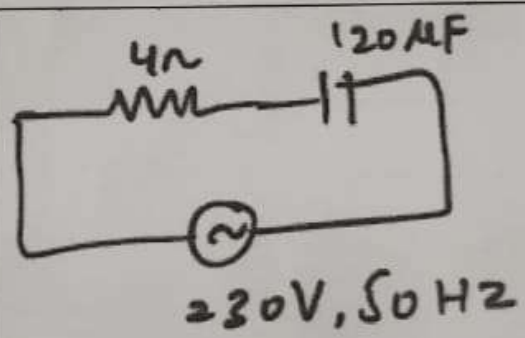
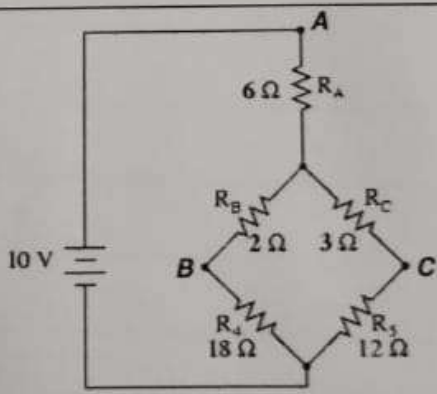


| Que | Statement/ Description | | RBL | MM | CO |
|-----|---|--|-----|----|-----|
| Q1 | Find the current through 2 ohms resistance using Superposition Theorem. |  | L2 | 5 | CO1 |
| Q2 | Reduce the following circuit into Thevenin's equivalent circuit? |  | L4 | 5 | CO1 |
| Q3 | Find the resultant resistance of the following circuit. |  | L2 | 5 | CO1 |
| Q4 | A 200kVA, 3500/250V, 50Hz, single phase transformer has 90 turns on the secondary winding. Assuming an ideal transformer, find i) primary and secondary currents, ii) max value of flux, ii) number of turns in the primary winding | | L3 | 5 | CO3 |
| Q5 | A series RC circuit having $R=4\Omega$ and $C=120\mu F$ is connected across 230 V, 50 Hz supply. Calculate (a) reactance (b) impedance (c) current drawn by circuit (d) power factor |  | L4 | 5 | CO2 |
| Q6 | Using Kirchhoff's voltage or current law find the voltage across $R_5=12$ ohms resistance. |  | L3 | 5 | CO |