

Section [Unit 4] 4 of 6


Question : 4 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

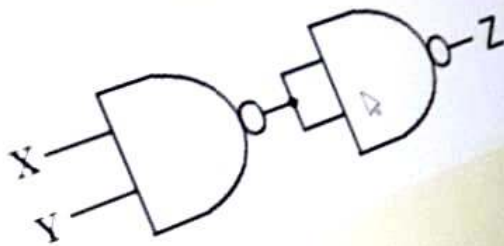The output (Z) of following digital logic circuit is



☐ X

☐ Y

☐ $X+Y$

☐ $X.Y$

Section [Unit 4] 4 of 6

Question : 7 of 10

Marks : 1

Negative Marks : -25% for wrong answer

Select the correct answer

Which of the following term is equivalent of the Boolean function $A(A + B)$

☐ A

☐ B

☐ A.B

☐ A+B

Finish

Clear Response



Section [Unit 4] 4 of 6

Question: 6 of 10

Marks: 1

Negative Marks: -25% on wrong answer

Select the correct answer

Which of the following is TRUE for n channel enhancement type MOSFET?

- ☐ For the n-channel enhancement MOSFET, a drain current will only flow when a gate voltage (V_{GS}) is applied to the gate terminal and the drain voltage (V_{DS}) is applied to the drain terminal.
- ☐ For the n-channel enhancement MOSFET, a drain current will only flow when a gate voltage (V_{GS}) is applied to the gate terminal and the drain voltage (V_{DS}) is applied to the drain terminal.
- ☐ For the n-channel enhancement MOSFET, a drain current will only flow when a gate voltage (V_{GS}) is applied to the gate terminal and the drain voltage (V_{DS}) is applied to the drain terminal.
- ☐ None of these

Final Answer

Clear Response



Section [Unit 4] 4 of 6

Question : 10 of 10

Marks : 1

Negative Marks : -20% on wrong answer

Select the correct answer

A family of logic gates that operates under the static discipline with the following voltage thresholds
 $V_{IL} = 1\text{ V}$, $V_{OL} = 0.5\text{ V}$, $V_{IH} = 3.5\text{ V}$, and $V_{OH} = 4.3\text{ V}$.
Determine the noise margins for logic 0.

☐ 0.1 V

☐ 0.5 V

☐ 1 V

☐ 1.5 V

Submit

Clear Response

Question [Unit 4] 4 of 6

Question : 9 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

When positive terminal of a battery is connected to an N side of PN junction diode and negative terminal of battery is connected to P side of PN junction diode then

- ☐ Holes and electrons tend to concentrate towards the junction
- ☐ Holes and electrons tend to move away from the junction
- ☐ depletion layer width decreases
- ☐ None of these

Finish

Clear Response

Section [Unit 5] 5 of 6


Question : 2 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

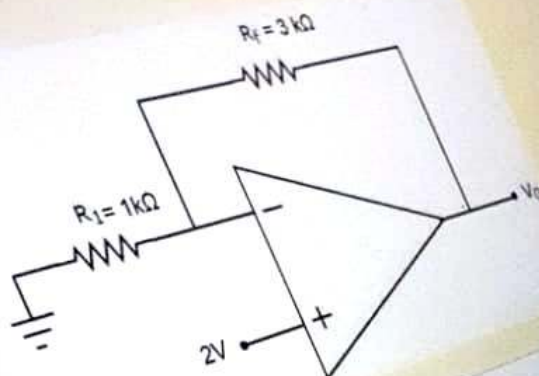In following circuit, the output voltage V_o is



☐ 2V

☐ 4V

☐ 8V

☐ 10V

Finish

Clear Response

Section [Unit 5] 5 of 6

Question : 5 of 10

Marks : 1

Negative Marks : 25% on wrong answer

Select the correct answer

Find the cut off frequency for an RC low pass filter of $R = 10 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$

☐ 99.25 Hz

☐ 159.15 Hz

☐ 219 Hz

☐ 239.35 Hz

Finish

Clear Response



Section [Unit 5] 5 of 6


Question : 7 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

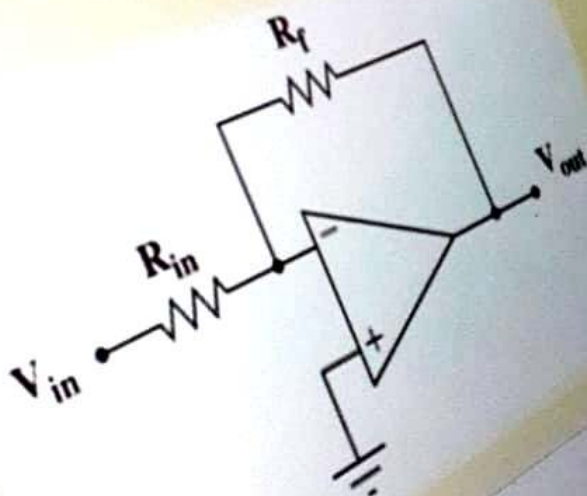In following circuit $R_{in} = 1\text{ k}\Omega$ and $R_f = 10\text{ k}\Omega$ then calculate the output voltage V_{out} if input voltage is 2 mV .



- ☐ 200 mV
- ☐ 250 mV
- ☐ -250 mV
- ☐ -200 mV

Section [Unit 5] 5 of 6


Question : 6 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

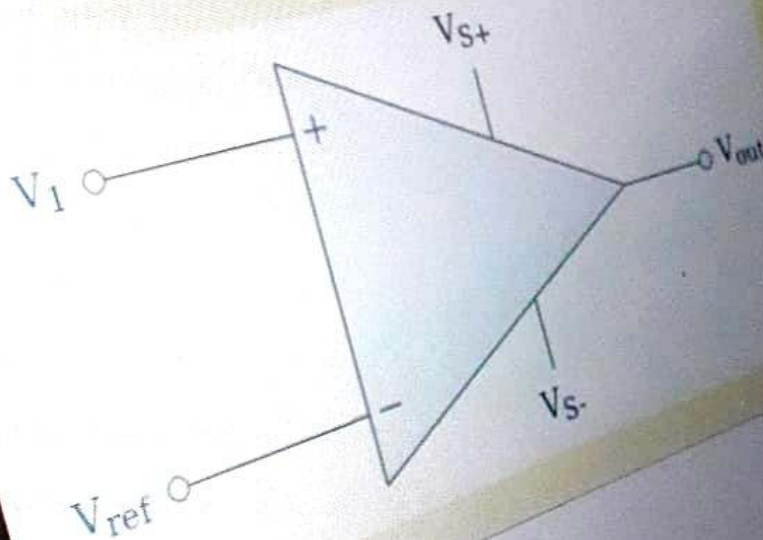In following ideal OP AMP based comparator, if $V_1 > V_{ref}$ then V_{out} will be



☐ V_{s-}

☐ V_{s+}

☐ 0

☐ V_1



Anywhere

Section [Unit 5] 5 of 6

Question : 10 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Which of the following statement is TRUE for a high pass filter.

- ☐ A high pass filter passes signals with a frequency lower than a selected cutoff frequency and attenuates signals with frequency above the cutoff frequency.
- ☐ A high pass filter passes signals with a frequency higher than a selected cutoff frequency and attenuates signals with frequency below the cutoff frequency.
- ☐ A high pass filter allows frequencies within a specific frequency range and rejects (attenuates) frequencies outside that range.
- ☐ A high pass filter rejects frequencies within a specific frequency range and allows frequencies outside that range.

Finish

Clear Response



Section [Unit 6] 6 of 6

Question : 3 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Which of the following statement is not TRUE?

- ☐ Digital signal processors are used in image processing systems
- ☐ Digital signal processors are used in audio and video processing systems
- ☐ Digital signal processors are used in telecommunication processing systems
- ☐ Digital signal processors does not used in image processing systems

Flash

Clear Response



Unit 6] 6 of 6

Question : 8 of 10

Marks : 1

Negative Marks : -25% on wrong answer

at the correct answer

Which of the following statement is true?

- ☐ RTOS and GPOS is used for time critical system
- ☐ RTOS and GPOS are used for systems/applications that are not time critical
- ☐ ARTOS is used for systems/applications that are not time critical whereas a GPOS is used for time critical systems
- ☐ A GPOS is used for systems/applications that are not time critical whereas an RTOS is used for time critical systems

Finish

Clear Response



Section [Unit 6] 6 of 6

Question : 9 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

In which operating system large memory is required?

- ☐ Real time operating system
- ☐ General purpose operating system
- ☐ Both real time and general purpose operating system
- ☐ None of these

Finish

Clear Response



Unit 5] 6 of 6

Question : 4 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Which of the following statement is true for a microprocessor?

- ☐ Microprocessor does not consists any Central Processing Unit
- ☐ Microprocessor consists of only a Central Processing Unit
- ☐ RAM is connected internally with Microprocessor
- ☐ All input and output devices are internally connected with Microprocessor

Finish

Clear Response

nit 6] 6 of 6

Question : 6 of 10

Marks : 1

Negative Marks : -25% on wrong answer

e correct answer

of the following statement is TRUE?

- ☐ Internet of Things (IoT) based system does not required any sensor and internet connectivity.
- ☐ Internet of Things (IoT) refers to a system of interrelated, internet-connected objects that are able to collect and transfer data over a wireless network within their operating range.
- ☐ Internet of Things (IoT) based wireless network need human intervention for monitoring and controlling the system.
- ☐ IOT based system can not be applicable for agriculture.

Finish

Clear Response

Section [Unit 6] 6 of 6

Question : 2 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Why microcontrollers are not called general purpose computers?

- ☐ because they consume low power
- ☐ because they have built in RAM and ROM
- ☐ because they are cheap
- ☐ because they have designed to perform dedicated task

Finish

Clear Response



in Anywhere

Section [Unit 5] 5 of 6

Question: 9 of 10

Marks: 1

Negative Marks: -25% on wrong answer

Select the correct answer

For OP AMP based integrator, which of the following component used for feedback connection?

- ☐ capacitor
- ☐ inductor
- ☐ diode
- ☐ MOSFET

Finish

Clear Response



Section [Unit 5] 5 of 6

Question : 8 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

The closed loop gain of a non inverting operational amplifier is usually

- ☐ zero
- ☐ more than 1
- ☐ less than 1
- ☐ None of these

Finish

Clear Response

Section [Unit 4] 4 of 6


Question : 6 of 10

Marks : 1

Negative Marks : 0.00, on wrong answer

Select the correct answer

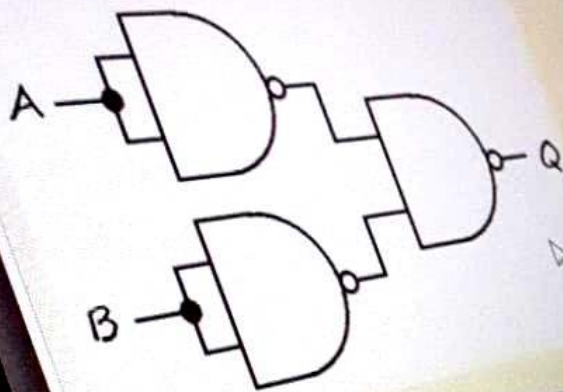The output of following digital logic circuit is



☐ $A.B$

☐ $A+B$

☐ $A.(A+B)$

☐ $B.(A+B)$

Clear Response

Final



Anywhere

tion [Unit 4] 4 of 6

Question : 2 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

A bipolar junction transistor operates with a collector current of 1.5 A and a base current of 50 mA. What will the emitter current be?

- ☐ 1.25 A
- ☐ 1.55 A
- ☐ 1.75 A
- ☐ 2 A

Finish

Clear Response



Section [Unit 4] 4 of 6

Question : 3 of 10

Marks : 1

Negative Marks : -25% for wrong answer

Select the correct answer

Which of the following statement is TRUE for Logic Gate?

- ☐ Fan-in defines the minimum number of digital inputs that a single logic gate can accept
- ☐ Fan-in defines the maximum number of digital inputs that a single logic gate can accept
- ☐ Fan-in defines the number of digital inputs are only two that a single logic gate can accept
- ☐ None of these

Finish

Clear Response

Select the correct answer

In OPAMP 741 IC, pin number 2 and 3 represents

- ☐ offset null terminals
- ☐ output terminal
- ☐ positive and negative voltage supply terminals
- ☐ Inverting and non inverting terminals

Finish 

Clear Response

Section [Unit 3] 3 of 6

Question : 4 of 5

Marks : 1

Negative Marks : -20% on wrong answer

Select the correct answer

An ideal transformer has a primary to secondary turns ratio of 3 : 25. If the load current is 6 A determine the primary current.

☐ 20 A

☐ 30 A

☐ 50 A

☐ 70 A

Finish

Clear Response



Section [Unit 6] 6 of 6

Question : 1 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Which of the following statement is TRUE?

- ☐ FPGA stands for Fixed Programmable Gate Arrays
- ☐ FPGA stands for Field Permanent Gate Arrays
- ☐ FPGA stands for Field Programmable Gate Access
- ☐ FPGA stands for Field Programmable Gate Arrays

Finish

Clear Response

[Unit 6] 6 of 6

Question: 7 of 10

Marks: 1

Negative Marks: -25% on wrong answer

the correct answer

Which of the following statements is true for FPGA?

- ☐ FPGA stands for First Programmable Gate Arrays
- ☐ FPGAs can not be reprogrammed to implement different logic functions
- ☐ FPGAs can be reprogrammed to implement different logic functions
- ☐ FPGA can not be configured to function as a processor

Finish

Clear Response



Section [Unit 6] 6 of 6

Question : 5 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Which of the following statement is TRUE?

- ☐ ASIC stands for application sensitive internet connection
- ☐ ASIC stands for application sensitive integrated circuit
- ☐ ASIC stands for application specific internet connection
- ☐ ASIC stands for application specific integrated circuit

Finish

Clear Response

Section [Unit 1] 1 of 6


Question : 5 of 5

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

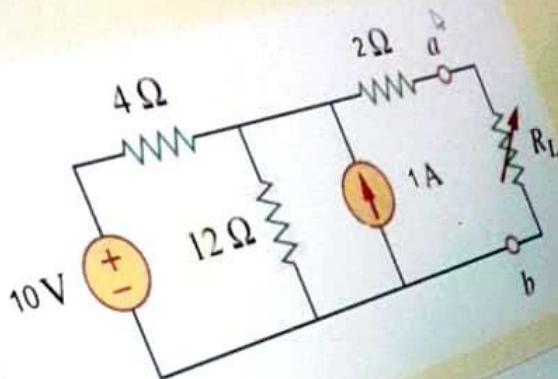In following circuit find the value of Thevenin resistance (R_{Th}) between the terminal a and b.



- ☐ 5 Ω
- ☐ 10 Ω
- ☐ 12 Ω
- ☐ 16 Ω

Clear Response



Section [Unit 2] 2 of 6


Question : 1 of 5

Marks : 1

Negative Marks : 0%

Select the correct answer

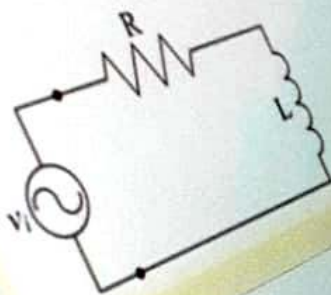In following circuit, the resistance of a resistor is $R = 25 \Omega$ and inductive reactance of an inductor is $X_L = 25 \Omega$. What is the value of power factor of the circuit if supply AC voltage is 230 V at 50 Hz ?



☐ 0.9

☐ 0.8

☐ 0.7

☐ 0.6

Next

Give Response

Section [Unit 6] 6 of 6

Question : 10 of 10

Marks : 1

Negative Marks : -25% on wrong answer

Select the correct answer

Microprocessor consume power compare to micro controller.

- ☐ less
- ☐ equal
- ☐ high
- ☐ none of the above

Finish 

Clear Response

in Anywhere.

on [Unit 5] 5 of 6

Question : 3 of 10

Marks : 1

Negative Marks : 25% on wrong answer

Select the correct answer

Which of the following statement is TRUE for a low pass filter.

- ☐ A low-pass filter passes signals with a frequency lower than a selected cutoff frequency and attenuates signals with frequencies higher than the cutoff frequency
- ☐ A low-pass filter attenuates signals with a frequency lower than a selected cutoff frequency and passes signals with frequencies higher than the cutoff frequency
- ☐ A low pass filter is allows frequencies within a specific frequency range and rejects (attenuates) frequencies outside that range
- ☐ A low pass filter is reject frequencies within a specific frequency range and allows frequencies outside that range

Finish

Clear Response

Select the correct answer

An ideal transformer has 600 primary turns and 1800 secondary turns. If the a.c. voltage applied across primary winding is 110 V then the voltage across secondary winding will be

- ☐ 230 V
- ☐ 270 V
- ☐ 300 V
- ☐ 330 V

Finish 

Clear Response

Section [Unit 2] 2 of 6


Question : 5 of 5

Marks : 1

Negative Marks : 25% on wrong answer

Select the correct answer

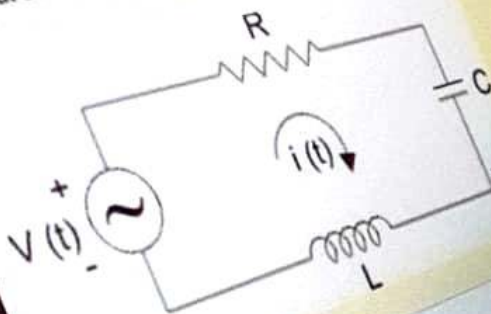In following circuit, the resistance of a resistor is $R = 15 \Omega$, capacitive reactance of capacitor is $X_C = 10 \Omega$ and inductive reactance of an inductor is $X_L = 2 \Omega$. What is the value of impedance of this circuit if supply AC voltage is 230 V at 50 Hz.



☐ 15Ω

☐ 16Ω

☐ 17Ω

☐ 18Ω

Clear Response